

LDL06E12A

LDLABO

2006年5月13日

1 論理譜

```
logicname LDL06E12A

procedure MEMORY
input RESET;
input CS;
input WP;
input DATAIN[4];
output DATAOUT[4];
bitr memory[4];

bitn memory6[4];
bitn memory7[4];
bitn ADDA0p;
bitn ADDA1p;
bitn ADDA2p;
bitn ADDA3p;
bitn ADDA4p;
bitn ADDA5p;
bitn ADDA6p;
bitn ADDA7p;

DATAOUT=memory;

if (RESET)
    memory=0;
else
    if (WP)
        if (CS)
            memory=DATAIN;
        else
            memory=memory;
    endif
else
    memory=memory;
endif
endif
endp

entity main
input RESET;
input ADDA[3];
input ADDB[3];
input ADDC[3];
input DATAIN[4];
input WP;
output DATABOUT[4];
output DATACOUT[4];

bitn memory0[4];
bitn memory1[4];
bitn memory2[4];
bitn memory3[4];
bitn memory4[4];
bitn memory5[4];

switch(ADDA)
    case 0: DATABOUT=memory0;
    case 1: DATABOUT=memory1;
    case 2: DATABOUT=memory2;
    case 3: DATABOUT=memory3;
    case 4: DATABOUT=memory4;
    case 5: DATABOUT=memory5;
    case 6: DATABOUT=memory6;
    case 7: DATABOUT=memory7;
endswitch

switch(ADDC)
    case 0: DATACOUT=memory0;
    case 1: DATACOUT=memory1;
    case 2: DATACOUT=memory2;
    case 3: DATACOUT=memory3;
    case 4: DATACOUT=memory4;
    case 5: DATACOUT=memory5;
    case 6: DATACOUT=memory6;
    case 7: DATACOUT=memory7;
endswitch

memory0=MEMORY(RESET,ADDA0p,WP,DATAIN);
memory1=MEMORY(RESET,ADDA1p,WP,DATAIN);
memory2=MEMORY(RESET,ADDA2p,WP,DATAIN);
memory3=MEMORY(RESET,ADDA3p,WP,DATAIN);
memory4=MEMORY(RESET,ADDA4p,WP,DATAIN);
memory5=MEMORY(RESET,ADDA5p,WP,DATAIN);
memory6=MEMORY(RESET,ADDA6p,WP,DATAIN);
memory7=MEMORY(RESET,ADDA7p,WP,DATAIN);

switch(ADDB)
    case 0: ADDA0p=1;
```

```

case 1: ADDA1p=1;
case 2: ADDA2p=1;
case 3: ADDA3p=1;
case 4: ADDA4p=1;
case 5: ADDA5p=1;
case 6: ADDA6p=1;
case 7: ADDA7p=1;
endswitch

ende

entity sim
output RESET;
output ADDA[3];
output ADDB[3];
output ADDC[3];
output DATAIN[4];
output WP;
output DATABOUT[4];
output DATACOUT[4];

bitr tc[8];

part main(RESET,ADDA,ADDB,ADDC
           ,DATAIN,WP
           ,DATABOUT,DATACOUT)

```

```

tc=tc+1;
if (tc<5) RESET=1; endif
switch(tc)
  case 10: ADDA=0; DATAIN=10; WP=1;
  case 11: ADDA=1; DATAIN=11; WP=1;
  case 12: ADDA=2; DATAIN=12; WP=1;
  case 13: ADDA=3; DATAIN=13; WP=1;
  case 14: ADDA=4; DATAIN=14; WP=1;
  case 15: ADDA=5; DATAIN=15; WP=1;
  case 16: ADDA=6; DATAIN=9; WP=1;
  case 17: ADDA=7; DATAIN=8; WP=1;
  case 20: ADDB=1; ADDC=7;
  case 21: ADDB=2; ADDC=6;
  case 22: ADDB=3; ADDC=5;
  case 23: ADDB=4; ADDC=4;
  case 24: ADDB=5; ADDC=3;
  case 25: ADDB=6; ADDC=2;
  case 26: ADDB=7; ADDC=1;
endswitch
ende
endlogic

```

2 動作

図 1 動作

